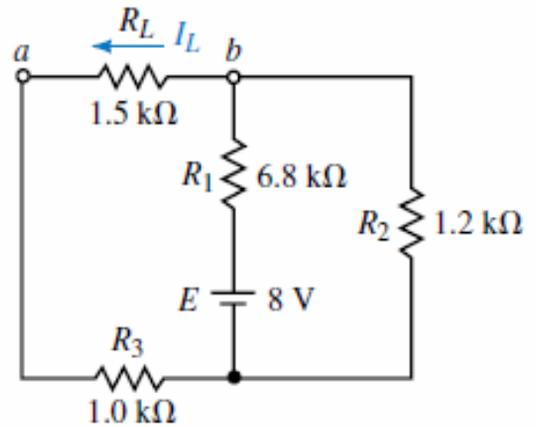


## Network Theorems (part2)

### Thévenin's Theorem

9) Find the Thévenin equivalent external to  $RL$  in circuit of Figure 9-83.. Use the equivalent circuit to find  $V_{ab}$ .




$$9. R_{Th} = 2.02 \text{ k}\Omega \quad E_{Th} = 1.20 \text{ V} \quad V_{ab} = -0.511 \text{ V}$$

11) Refer to the circuit of Figure 9–85:

a. Find the Thévenin equivalent circuit external to  $RL$ .

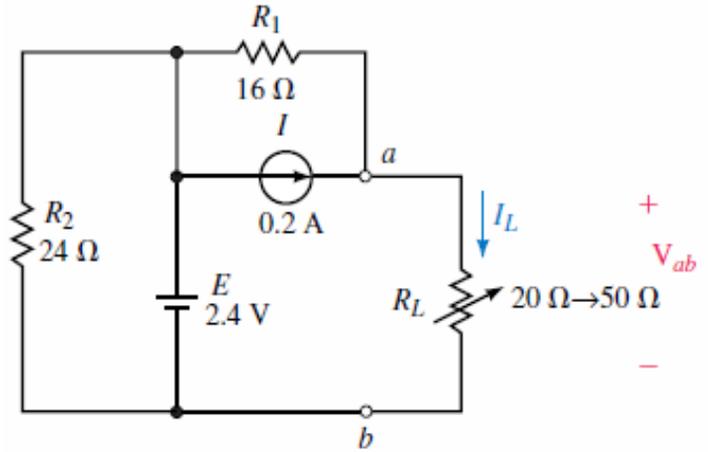b. Use the equivalent circuit to determine  $V_{ab}$  when  $RL = 20 \Omega$  and when  $RL = 50 \Omega$ .




11. a.  $R_{Th} = 16 \Omega$   $E_{Th} = 5.6 \text{ V}$

b. When  $R_L = 20 \Omega$ :  $V_{ab} = 3.11 \text{ V}$

When  $R_L = 50 \Omega$ :  $V_{ab} = 4.24 \text{ V}$

13) Refer to the circuit of Figure 9–87:

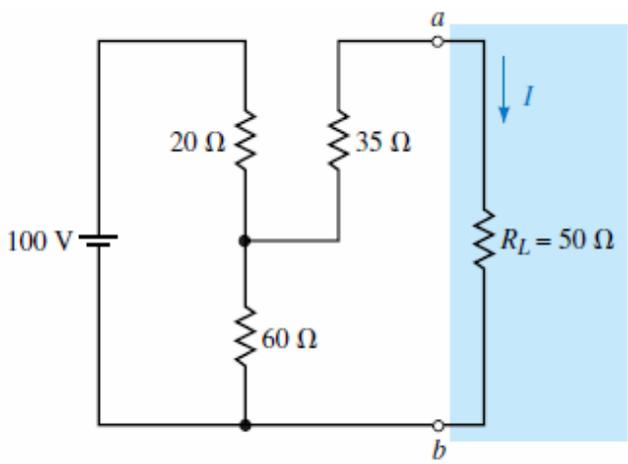- a. Find the Thévenin equivalent circuit external to the indicated terminals.
- b. Use the Thévenin equivalent circuit to determine the current through the indicated branch.




13. a.  $E_{Th} = 75\text{ V}$   $R_{Th} = 50\ \Omega$   
b.  $I = 0.75\text{ A}$

17) Refer to the circuit of Figure 9–91:

a. Find the Thévenin equivalent circuit external to  $RL$ .

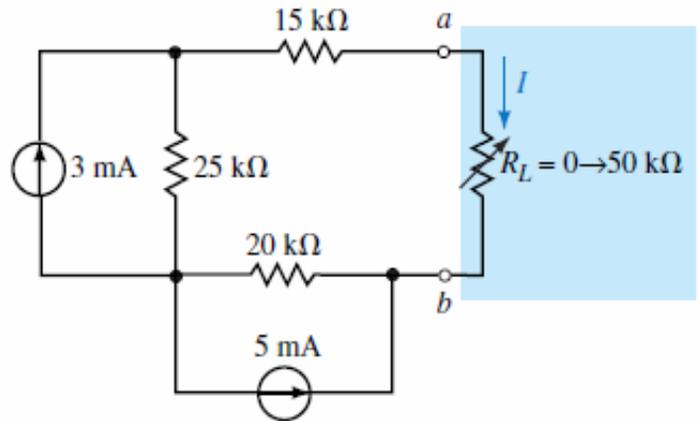
b. Use the Thévenin equivalent circuit to find the current  $I$  when  $RL = 0$ ,  $10\text{ k}\Omega$ , and  $50\text{ k}\Omega$ .



- |        |                              |                        |
|--------|------------------------------|------------------------|
| 17. a. | $R_{Th} = 60\text{ k}\Omega$ | $E_{Th} = 25\text{ V}$ |
| b.     | $R_L = 0:$                   | $I = -0.417\text{ mA}$ |
|        | $R_L = 10\text{ k}\Omega:$   | $I = -0.357\text{ mA}$ |
|        | $R_L = 50\text{ k}\Omega:$   | $I = -0.227\text{ mA}$ |

## Norton's Theorem

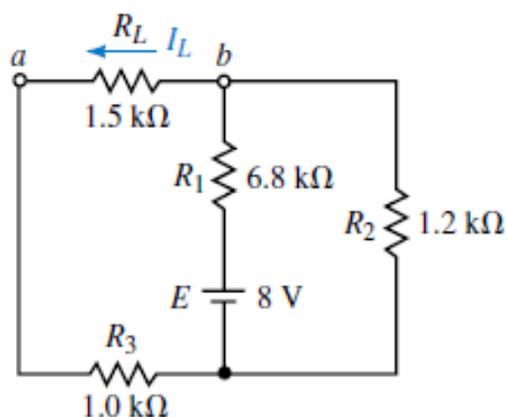
27) Find the Norton equivalent circuit external to  $R_L$  in the circuit of the Figure . Use the equivalent circuit to find  $I_L$  for the circuit.



$$27. I_N = 0.594\text{ mA}, \quad R_N = 2.02\text{ k}\Omega, \quad I_L = 0.341\text{ mA}$$

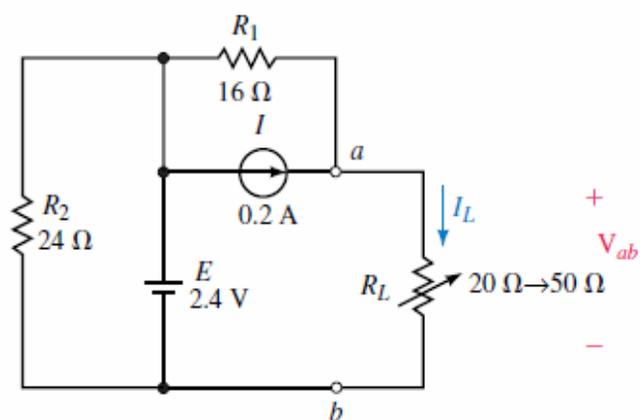29. Refer to the circuit of Figure 9–85:

- Find the Norton equivalent circuit external to  $R_L$ .
- Use the equivalent circuit to determine  $I_L$  when  $R_L = 20\ \Omega$  and when  $R_L = 50\ \Omega$ .




29. a.  $I_N = 0.35\ \text{A}$ ,  $R_N = 16\ \Omega$

b.  $R_L = 20\ \Omega$ :  $I_L = 0.156\ \text{A}$

$R_L = 50\ \Omega$ :  $I_L = 0.085\ \text{A}$

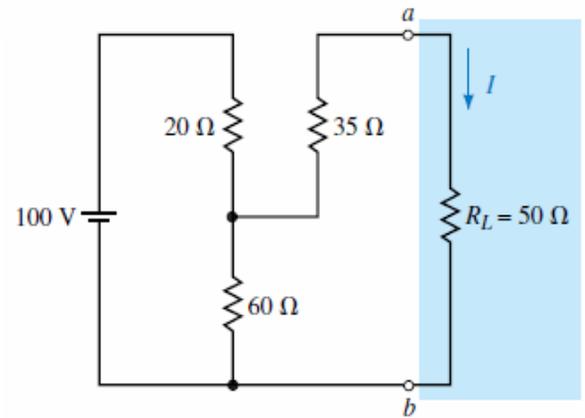31. a. Find the Norton equivalent circuit external to the indicated terminals of Figure 9–87.
- b. Convert the Thévenin equivalent circuit of Problem 13 to its Norton equivalent.




31. a.  $I_N = 1.50 \text{ A}$ ,  $R_N = 50 \Omega$

b.  $I_N = 1.50 \text{ A}$ ,  $R_N = 50 \Omega$



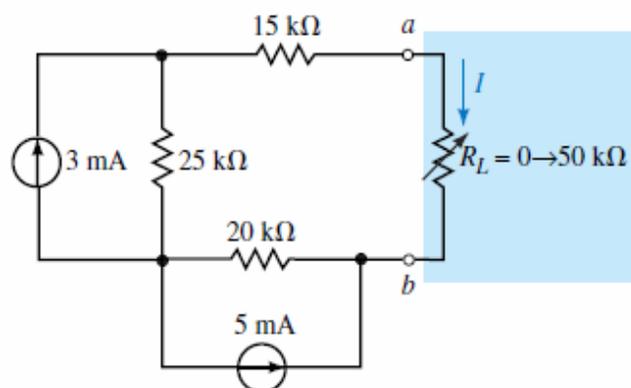33. Repeat Problem 31 for the circuit of Figure 9–91.



33. a.  $I_N = 0.417 \text{ mA}$ ,  $R_N = 60 \text{ k}\Omega$   
b.  $I_N = 0.417 \text{ mA}$ ,  $R_N = 60 \text{ k}\Omega$